

MODEL ANSWER
WINTER- 18 EXAMINATION

Subject Title: Digital Techniques

Subject Code:

22320

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more Importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q.N.	Answer	Marking Scheme
Q.1		Attempt any FIVE of the following :	Total Marks 10
	a)	Write the radix of binary,octal,decimal and hexadecimal number system.	2M
	Ans:	Radix of: Binary – 2 Octal - 8 Decimal - 10 Hexadecimal -16	½ M each
	b)	Draw the circuit diagram for AND and OR gates using diodes.	2M
	Ans:	<p><u>Diode AND gate :Diode OR gate :</u></p>	1 M each



OUR CENTERS :


KALYAN | DOMBIVLI | THANE | NERUL | DADAR



Contact - 9136008228

c)	Write simple example of Boolean expression for SOP and POS.	2M
Ans:	<p>SOP form:</p> $Y = AB + BC + A\bar{C}$ <p>POS form:</p> $Y = (A + B)(B + C)(A + \bar{C})$	1 M each (any proper example can be considered)
d)	State the necessity of multiplexer.	2M
Ans:	<p>Necessity of Multiplexer:</p> <ul style="list-style-type: none"> • It reduces the number of wires required to pass data from source to destination. • For minimizing the hardware circuit. • For simplifying logic design. • In most digital circuits, many signals or channels are to be transmitted, and then it becomes necessary to send the data on a single line simultaneously. • Reduces the cost as sending many signals separately is expensive and requires more wires to send. 	2 M(any two proper points)
e)	Draw logic diagram of T flip-flop and give its truth table.	2M
Ans:	<p>Note: Diagram Using logic gates with proper connection also can be consider.</p> <p>Logic Diagram:</p>	1M (any one diagram) 1 M

	<p>Truth Table:</p> <table border="1"> <thead> <tr> <th>Input T_n</th> <th>Output Q_{n+1}</th> <th>Operation Performed</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>Q_n</td> <td>No change</td> </tr> <tr> <td>1</td> <td>\bar{Q}_n</td> <td>Toggle</td> </tr> </tbody> </table>	Input T_n	Output Q_{n+1}	Operation Performed	0	Q_n	No change	1	\bar{Q}_n	Toggle																	
Input T_n	Output Q_{n+1}	Operation Performed																									
0	Q_n	No change																									
1	\bar{Q}_n	Toggle																									
f)	Define modulus of a counter. Write the numbers of flip flops required for Mod-6 counter.	2M																									
Ans:	<ul style="list-style-type: none"> Modulus of counter is defined as number of states/clock the counter counts. The numbers of flip flops required for Mod-6 counter is 3. 	Definition: 1 M No. of FF- 1M																									
g)	State function of preset and clear in flip flop.	2M																									
Ans:	<ul style="list-style-type: none"> In the flip flop , when the power is switched on, the state of the circuit is uncertain i.e. may be $Q = 1$ or $Q = 0$. Hence, the function of preset is to set a flip flop i.e. $Q = 1$ and the function of clear is to clear a flip flop i.e. $Q = 0$. <table border="1"> <thead> <tr> <th colspan="3">Inputs</th> <th>Output</th> <th>Operation performed</th> </tr> <tr> <th>CK</th> <th>Cr</th> <th>Pr</th> <th>Q</th> <th></th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>1</td> <td>Q_{n+1} (Table 7.1)</td> <td>Normal FLIP-FLOP</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>Clear</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>1</td> <td>Preset</td> </tr> </tbody> </table>	Inputs			Output	Operation performed	CK	Cr	Pr	Q		1	1	1	Q_{n+1} (Table 7.1)	Normal FLIP-FLOP	0	0	1	0	Clear	0	1	0	1	Preset	1 M for each function (table is optional)
Inputs			Output	Operation performed																							
CK	Cr	Pr	Q																								
1	1	1	Q_{n+1} (Table 7.1)	Normal FLIP-FLOP																							
0	0	1	0	Clear																							
0	1	0	1	Preset																							

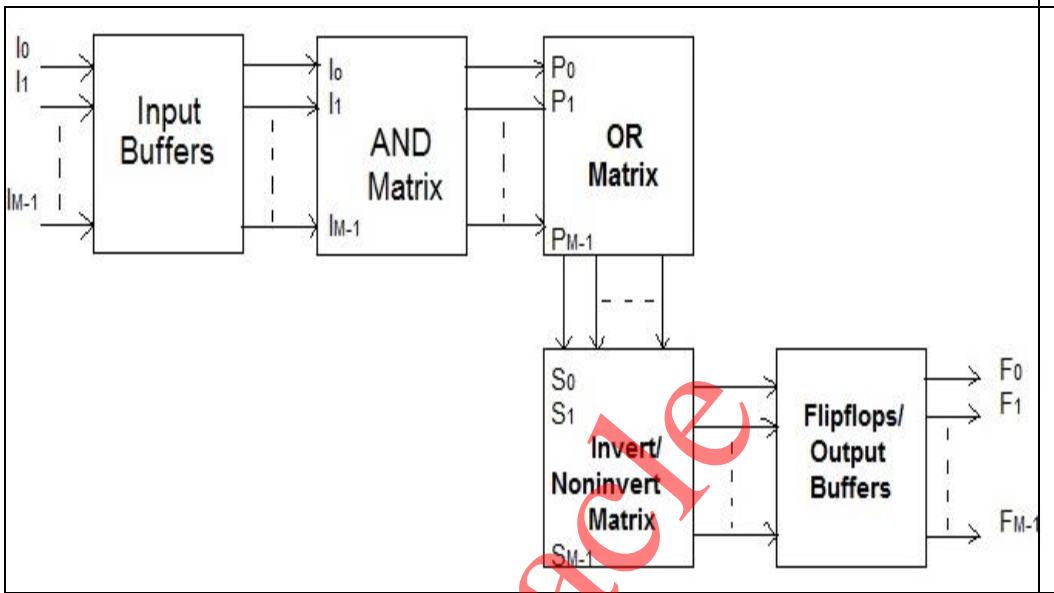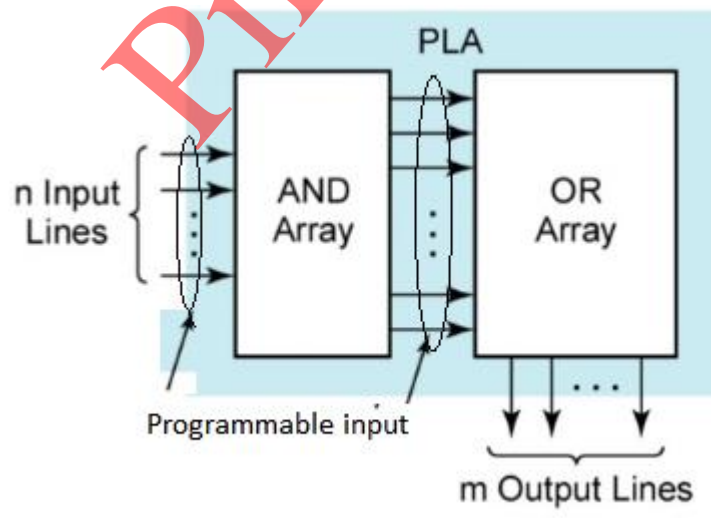Q 2	Attempt any THREE of the following :	12-Total Marks
a)	Draw the block diagram of Programmable Logic Array.	4M
Ans:	<p>Diagram :-</p>  <p style="text-align: center;">Block diagram of Programmable Logic Array</p> <p style="text-align: center;">OR</p> 	4 M

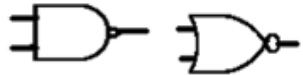b)	<p>Convert – $(255)_{10} = (?)_{16} = (?)_8$ $(157)_{10} = (?)_{BCD} = (?)_{\text{Excess3}}$</p>	4M																																										
Ans:	<p>(i) $(255)_{10} = (FF)_{16} = (377)_8$</p> <p>$(255)_{10} = (FF)_{16}$</p> <table style="margin-left: 20px;"> <tr> <td style="border-right: 1px solid black; padding-right: 5px;">16</td> <td style="border-bottom: 1px solid black; padding: 0 5px;">255</td> <td style="padding: 0 5px;">F (15)</td> <td rowspan="3" style="vertical-align: middle; padding-left: 10px;">↑</td> </tr> <tr> <td style="border-right: 1px solid black; padding-right: 5px;"></td> <td style="border-bottom: 1px solid black; padding: 0 5px;">15</td> <td style="padding: 0 5px;">F</td> </tr> <tr> <td style="border-right: 1px solid black; padding-right: 5px;"></td> <td style="padding: 0 5px;"></td> <td style="padding: 0 5px;"></td> </tr> </table> <p>$(255)_{10} = (377)_8$</p> <table style="margin-left: 20px;"> <tr> <td style="border-right: 1px solid black; padding-right: 5px;">8</td> <td style="border-bottom: 1px solid black; padding: 0 5px;">255</td> <td style="padding: 0 5px;">7</td> <td rowspan="3" style="vertical-align: middle; padding-left: 10px;">↑</td> </tr> <tr> <td style="border-right: 1px solid black; padding-right: 5px;">8</td> <td style="border-bottom: 1px solid black; padding: 0 5px;">31</td> <td style="padding: 0 5px;">7</td> </tr> <tr> <td style="border-right: 1px solid black; padding-right: 5px;"></td> <td style="padding: 0 5px;">3</td> <td style="padding: 0 5px;">3</td> </tr> </table> <p>(ii) $(157)_{10} = (000101010111)_{BCD} = (010010001010)_{\text{Excess3}}$</p> <p>$(157)_{10} = (000101010111)_{BCD}$</p> <table style="margin-left: 40px;"> <tr> <td style="text-align: center; padding: 0 5px;"><u>1</u></td> <td style="text-align: center; padding: 0 5px;"><u>5</u></td> <td style="text-align: center; padding: 0 5px;"><u>7</u></td> </tr> <tr> <td style="text-align: center; padding: 0 5px;">0001</td> <td style="text-align: center; padding: 0 5px;">0101</td> <td style="text-align: center; padding: 0 5px;">0111</td> </tr> </table> <p>$(000101010111)_{BCD} = (010010001010)_{\text{Excess3}}$</p> <table style="margin-left: 40px;"> <tr> <td style="padding: 0 5px;"></td> <td style="padding: 0 5px;">11</td> <td style="padding: 0 5px;">111</td> <td style="padding: 0 5px;">111</td> </tr> <tr> <td style="padding: 0 5px;"></td> <td style="padding: 0 5px;">0001</td> <td style="padding: 0 5px;">0101</td> <td style="padding: 0 5px;">0111</td> </tr> <tr> <td style="padding: 0 5px;">+</td> <td style="padding: 0 5px;">0011</td> <td style="padding: 0 5px;">0011</td> <td style="padding: 0 5px;">0011</td> </tr> <tr> <td style="padding: 0 5px;"></td> <td style="padding: 0 5px;">0100</td> <td style="padding: 0 5px;">1000</td> <td style="padding: 0 5px;">1010</td> </tr> </table>	16	255	F (15)	↑		15	F				8	255	7	↑	8	31	7		3	3	<u>1</u>	<u>5</u>	<u>7</u>	0001	0101	0111		11	111	111		0001	0101	0111	+	0011	0011	0011		0100	1000	1010	<p>1 M</p> <p>1 M</p> <p>1 M</p> <p>1 M</p>
16	255	F (15)	↑																																									
	15	F																																										
8	255	7	↑																																									
8	31	7																																										
	3	3																																										
<u>1</u>	<u>5</u>	<u>7</u>																																										
0001	0101	0111																																										
	11	111	111																																									
	0001	0101	0111																																									
+	0011	0011	0011																																									
	0100	1000	1010																																									
c)	<p>Draw the symbol, truth table and logic expression of any one universal logic gate. Write reason why it is called universal gate.</p>	4M																																										
Ans:	<p><u>(Note: Any one universal gate has to be considered.)</u></p> <p>Universal Gates: NAND or NOR Symbol:</p> <div style="text-align: center;">  </div> <p>Truth table:</p> <table style="margin-left: 20px;"> <tr> <td style="border: 1px solid black; padding: 2px;">A</td> <td style="border: 1px solid black; padding: 2px;">B</td> <td style="border: 1px solid black; padding: 2px;">Y</td> <td style="border: 1px solid black; padding: 2px;">A</td> <td style="border: 1px solid black; padding: 2px;">B</td> <td style="border: 1px solid black; padding: 2px;">Y</td> </tr> <tr> <td style="border: 1px solid black; padding: 2px;">0</td> <td style="border: 1px solid black; padding: 2px;">0</td> <td style="border: 1px solid black; padding: 2px;">1</td> <td style="border: 1px solid black; padding: 2px;">0</td> <td style="border: 1px solid black; padding: 2px;">0</td> <td style="border: 1px solid black; padding: 2px;">1</td> </tr> <tr> <td style="border: 1px solid black; padding: 2px;">0</td> <td style="border: 1px solid black; padding: 2px;">1</td> <td style="border: 1px solid black; padding: 2px;">1</td> <td style="border: 1px solid black; padding: 2px;">0</td> <td style="border: 1px solid black; padding: 2px;">1</td> <td style="border: 1px solid black; padding: 2px;">0</td> </tr> <tr> <td style="border: 1px solid black; padding: 2px;">1</td> <td style="border: 1px solid black; padding: 2px;">0</td> <td style="border: 1px solid black; padding: 2px;">1</td> <td style="border: 1px solid black; padding: 2px;">1</td> <td style="border: 1px solid black; padding: 2px;">0</td> <td style="border: 1px solid black; padding: 2px;">0</td> </tr> <tr> <td style="border: 1px solid black; padding: 2px;">1</td> <td style="border: 1px solid black; padding: 2px;">1</td> <td style="border: 1px solid black; padding: 2px;">0</td> <td style="border: 1px solid black; padding: 2px;">1</td> <td style="border: 1px solid black; padding: 2px;">1</td> <td style="border: 1px solid black; padding: 2px;">0</td> </tr> </table> <p>Logic expression:</p> <p style="text-align: center;">$Y = \overline{A \cdot B}$ $Y = \overline{A + B}$</p> <p>NAND and NOR gates are called as “Universal Gate” as it is possible to implement any Boolean expression using these gates.</p>	A	B	Y	A	B	Y	0	0	1	0	0	1	0	1	1	0	1	0	1	0	1	1	0	0	1	1	0	1	1	0	<p>1 M</p> <p>1 M</p> <p>1 M</p> <p>1 M</p>												
A	B	Y	A	B	Y																																							
0	0	1	0	0	1																																							
0	1	1	0	1	0																																							
1	0	1	1	0	0																																							
1	1	0	1	1	0																																							

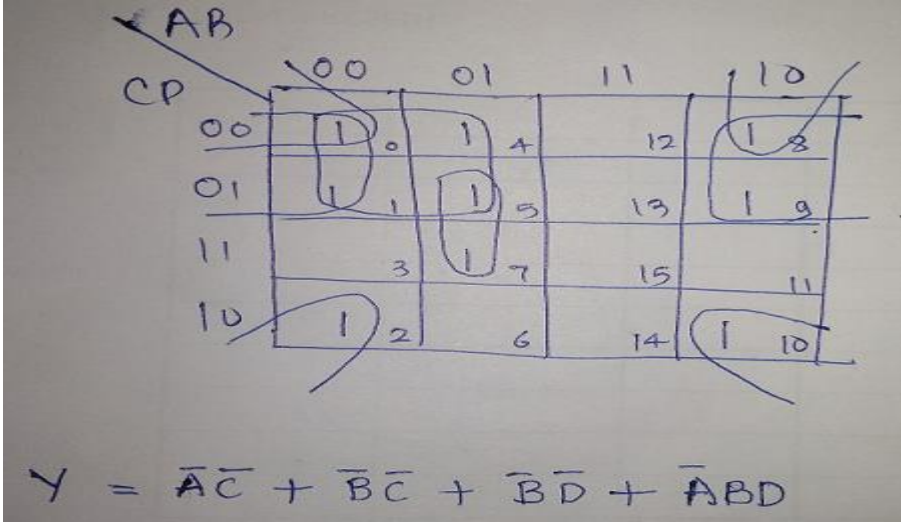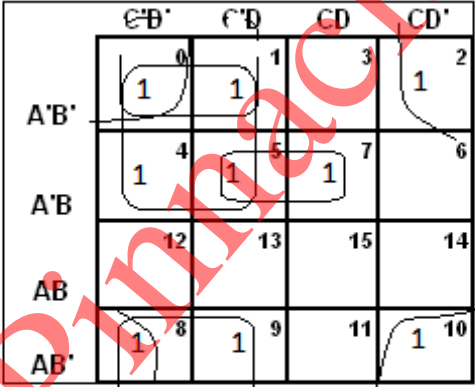	<p>d) Minimize the following expression using K-Map. $f(A, B, C, D) = \sum m (0, 1, 2, 4, 5, 7, 8, 9, 10)$</p>	4M
Ans:	 <p style="text-align: center;">OR</p>  <p style="text-align: center;">$\bar{A}\bar{C} + \bar{B}\bar{C} + \bar{B}\bar{D} + \bar{A}BD$</p>	<p>1 M – drawing k map 1 M – Representing function in k map 1 M – Grouping 1M – Final expression</p>


Q. 3		<p>Attempt any THREE:</p>	12-Total Marks															
	<p>a)</p>	<p>Compare TTL and CMOS logic families on the basis of following:</p> <ul style="list-style-type: none"> (i) Propagation delay (ii) Power Dissipation (iii) Fan-out (iv) Basic gate 	4M															
	<p>Ans:</p>	<p style="text-align: center;"><u>NOTE :- (Relevant points of comparison- 1 M for each point)</u></p> <table border="1" style="width: 100%; border-collapse: collapse; margin: 10px 0;"> <thead> <tr> <th style="width: 30%;">Parameter</th> <th style="width: 35%;">CMOS</th> <th style="width: 35%;">TTL</th> </tr> </thead> <tbody> <tr> <td>Propagation delay</td> <td>70-105 nsec/more than TTL</td> <td>10 nsec/Less than CMOS</td> </tr> <tr> <td>Power Dissipation</td> <td>Less 0.1 mW/Less than TTL</td> <td>More 10 mW/ More than CMOS</td> </tr> <tr> <td>Fan-out</td> <td>50/More than TTL</td> <td>10/Less than CMOS</td> </tr> <tr> <td>Basic gate</td> <td>NAND/NOR</td> <td>NAND</td> </tr> </tbody> </table>	Parameter	CMOS	TTL	Propagation delay	70-105 nsec/more than TTL	10 nsec/Less than CMOS	Power Dissipation	Less 0.1 mW/Less than TTL	More 10 mW/ More than CMOS	Fan-out	50/More than TTL	10/Less than CMOS	Basic gate	NAND/NOR	NAND	1 Marks each point
Parameter	CMOS	TTL																
Propagation delay	70-105 nsec/more than TTL	10 nsec/Less than CMOS																
Power Dissipation	Less 0.1 mW/Less than TTL	More 10 mW/ More than CMOS																
Fan-out	50/More than TTL	10/Less than CMOS																
Basic gate	NAND/NOR	NAND																
	<p>b)</p>	<p>Describe the function of full Adder Circuit using its truth table, K-Map simplification and logic diagram.</p>	4M															
	<p>Ans:</p>	<p>(Diagram- 1M,Truth table-1M, K-map- 1M,Logic diagram-1 M)</p> <p>A full adder is a combinational logic circuit that performs addition between three bits, the two input bits A and B, and carry C from the previous bit.</p> <p><u>Block diagram :</u></p> <div style="text-align: center; margin: 10px 0;"> </div>	1M															
			1M															

Truth Table :

Input			Output	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

1M


K-Map :-

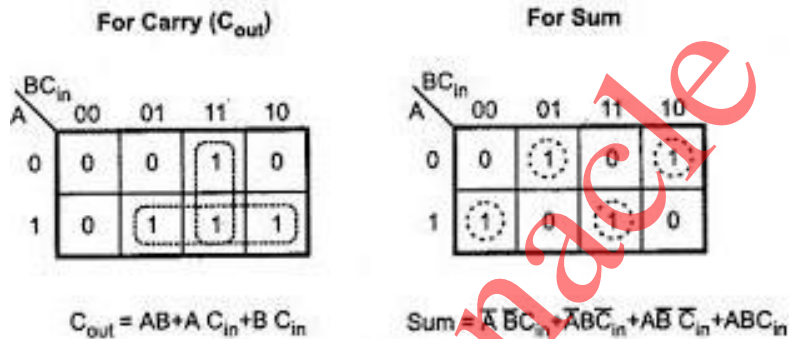

1M

Logic Diagram:

 (Note: Logic Diagram using basic or universal gate also can be consider)




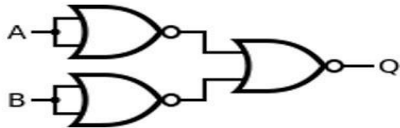
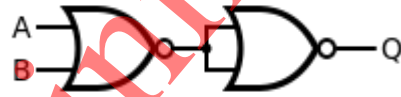
 
c)	<p>Realize the basic logic gates, NOT, OR and AND gates using NOR gates only.</p>	4M																				
Ans:	<p>(NOT GATE USING NOR GATE:1 M)</p>	1M																				
<p style="text-align: center;">  </p> <p>where, $X = A \text{ NOR } A$ $x = \bar{A}$</p>																						
<p>(AND GATE USING NOR GATE:1.5 MARKS)</p>																						
<p style="text-align: center;">  </p>																						
<p>$\overline{\overline{A+B}} = \overline{\bar{A} + \bar{B}} = \bar{A} \cdot \bar{B}$ $\overline{\bar{A} + \bar{B}} = \bar{A} \cdot \bar{B}$ $\overline{\bar{A} + \bar{B}} = \bar{A} \cdot \bar{B}$</p>																						
<p>(OR GATE USING NOR GATE:1.5 MARKS)</p>																						
<p style="text-align: center;">  </p> <p>$\overline{\overline{A+B}} = \overline{\bar{A} \cdot \bar{B}} = A + B$ $\overline{\bar{A} \cdot \bar{B}} = A + B$</p>																						
d)	<p>Describe the working of JK flip-flop with its truth table and logic diagram.</p>	4M																				
Ans:	<p><i>(Diagram-2 M, Working-1M, Truth table-1M)</i></p>	1M																				
<p>Truth Table :-</p>																						
<p style="text-align: center;"> Truth Table </p> <table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>J</th> <th>K</th> <th>CLK</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>↑</td> <td>Q_0 (no change)</td> </tr> <tr> <td>1</td> <td>0</td> <td>↑</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>↑</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>↑</td> <td>\bar{Q}_0 (toggles)</td> </tr> </tbody> </table>			J	K	CLK	Q	0	0	↑	Q_0 (no change)	1	0	↑	1	0	1	↑	0	1	1	↑	\bar{Q}_0 (toggles)
J	K	CLK	Q																			
0	0	↑	Q_0 (no change)																			
1	0	↑	1																			
0	1	↑	0																			
1	1	↑	\bar{Q}_0 (toggles)																			

Diagram :-



2M

Working :-

The **JK flip flop** is basically a gated SR flip-flop with the addition of a clock input circuitry that prevents the illegal or invalid output condition that can occur when both inputs S and R are equal to logic level “1”. Due to this additional clocked input, a JK flip-flop has four possible input combinations, “logic 1”, “logic 0”, “no change” and “toggle”.

1M

Both the S and the R inputs of the previous SR bistable have now been replaced by two inputs called the J and K inputs, respectively after its inventor Jack Kilby. Then this equates to: $J = S$ and $K = R$.

The two 2-input AND gates of the gated SR bistable have now been replaced by two 3-input NAND gates with the third input of each gate connected to the outputs at Q and \bar{Q} . This cross coupling of the SR flip-flop allows the previously invalid condition of $S = “1”$ and $R = “1”$ state to be used to produce a “toggle action” as the two inputs are now interlocked.

If the circuit is now “SET” the J input is inhibited by the “0” status of Q through the lower NAND gate. If the circuit is “RESET” the K input is inhibited by the “0” status of \bar{Q} through the upper NAND gate. As Q and \bar{Q} are always different we can use them to control the input. When both inputs J and K are equal to logic “1”, the JK flip flop toggles


Q. 4	A)	Attempt any THREE of the following:	12-Total Marks
	a)	Draw and explain working of 4 bit serial Input parallel Output shift register.	4M
	Ans:	<p>(Diagram:2M,Explanation:2M)</p> <p>Diagram :-</p> <p>Explanation :-</p> <p>If a logic “1” is connected to the DATA input pin of FFA then on the first clock pulse the output of FFA and therefore the resulting Q_A will be set HIGH to logic “1” with all the other outputs still remaining LOW at logic “0”.</p> <p>Assume now that the DATA input pin of FFA has returned LOW again to logic “0” giving us one data pulse or 0-1-0.</p> <p>The second clock pulse will change the output of FFA to logic “0” and the output of FFB and Q_B HIGH to logic “1” as its input D has the logic “1” level on it from Q_A. The logic “1” has now moved or been “shifted” one place along the register to the right as it is now at Q_A.</p> <p>When the third clock pulse arrives this logic “1” value moves to the output of FFC (Q_C) and so on until the arrival of the fifth clock pulse which sets all the outputs Q_A to Q_D back again to logic level “0” because the input to FFA has remained constant at logic level “0”.</p> <p>The effect of each clock pulse is to shift the data contents of each stage one place to the right, and this is shown in the following table until the complete data value of 0-0-0-1 is stored in the register. This data value can now be read directly from the outputs of Q_A to Q_D.</p> <p>Then the data has been converted from a serial data input signal to a parallel data output. The truth table and following waveforms show the propagation of the logic “1” through the register from left to right as follows.</p> <p>Basic Data Movement Through A Shift Register</p>	<p>2M</p> <p>2M</p>

Clock Pulse No	QA	QB	QC	QD
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	0	0	0	0

b) Draw 16:1 MUX tree using 4:1 MUX.

4M

Ans: Diagram :-

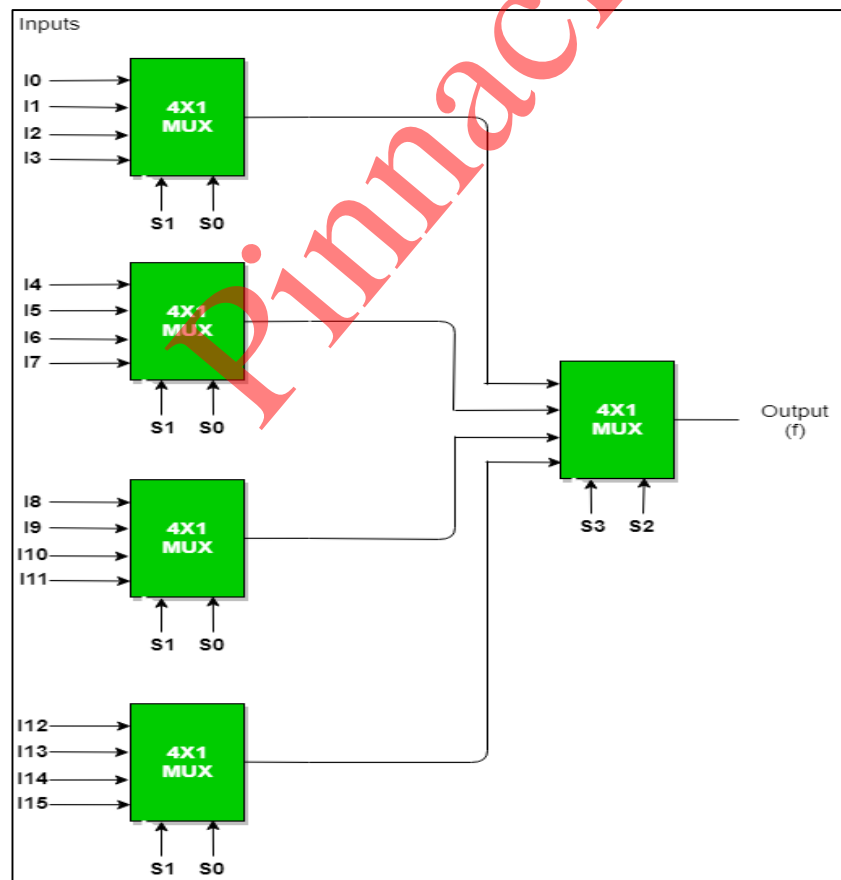

4M



	<p>c) Calculate analog output of 4 bit DAC for digital input 1101. Assume $V_{FS} = 5V$.</p>	4M
	<p>Ans: (Formula- 1M, Correct problem solving- 3M)</p> <p>Formula :-</p> <p>$V_R = V_{FS}$</p> <div style="background-color: #e0e0e0; padding: 5px; border: 1px solid #ccc; display: inline-block;"> $V_o = V_R [d_1 2^{-1} + d_2 2^{-2} + \dots + d_n 2^{-n}]$ </div> <p style="text-align: center;">3M</p> $= 5(1 \times 2^{-1} + 1 \times 2^{-2} + 0 \times 2^{-3} + 1 \times 2^{-4})$ $= 5(0.5 + 0.25 + 0 + 0.0625)$ $= 4.0625 \text{ Volts}$ <p style="text-align: center;">OR</p> $V_{FS} = V_R \cdot \left(\frac{b_3}{2} + \frac{b_2}{4} + \frac{b_1}{8} + \frac{b_0}{16} \right)$ <p>Note – (Since V_R is not given find V_R)</p> <p>Full Scale o/p mean</p> <p>$b_3 b_2 b_1 b_0 = 1111$</p> <p>$V_{FS} = 5V$</p> $5 = V_R \cdot \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} \right)$ <p>$V_R = 5.33$</p> <p>For digital i/p $b_3 b_2 b_1 b_0 = 1101$</p> $V_o = 5.33 \left(\frac{1}{2} + \frac{1}{4} + \frac{0}{8} + \frac{1}{16} \right)$ <p>$V_o = 4.33V$</p>	<p>1M</p> <p>3M</p> <p>2 Marks for V_R and 2 marks for V_o</p>
	<p>d) State De Morgan's theorem and prove any one.</p>	4M
	<p>Ans: (Each State and proof using table- 2M each)</p>	2M



i) $\overline{AB} = \overline{A} + \overline{B}$

It states that compliment of product is equal to sum of their compliments.

1	2	3	4	5	6
A	B	\overline{AB}	\overline{A}	\overline{B}	$\overline{A+B}$
0	0	1	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0

Column 03 = column 06

i.e. $\overline{AB} = \overline{A} + \overline{B}$

Hence proved

2M

OR

ii) $\overline{A+B} = \overline{A} \cdot \overline{B}$

It states that complement of sum is equal to product of their complements.

1	2	3	4	5	6
A	B	$\overline{A+B}$	\overline{A}	\overline{B}	$\overline{A \cdot B}$
0	0	1	1	1	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	0

Column 03 = column 06

$\therefore \overline{A+B} = \overline{A} \cdot \overline{B}$


Hence proved.

e) Design one digit BCD Adder using IC 7483

Ans: (Diagram:4M)

(Note: Labeled combinational circuit can be drawn using universal gate also)

4M

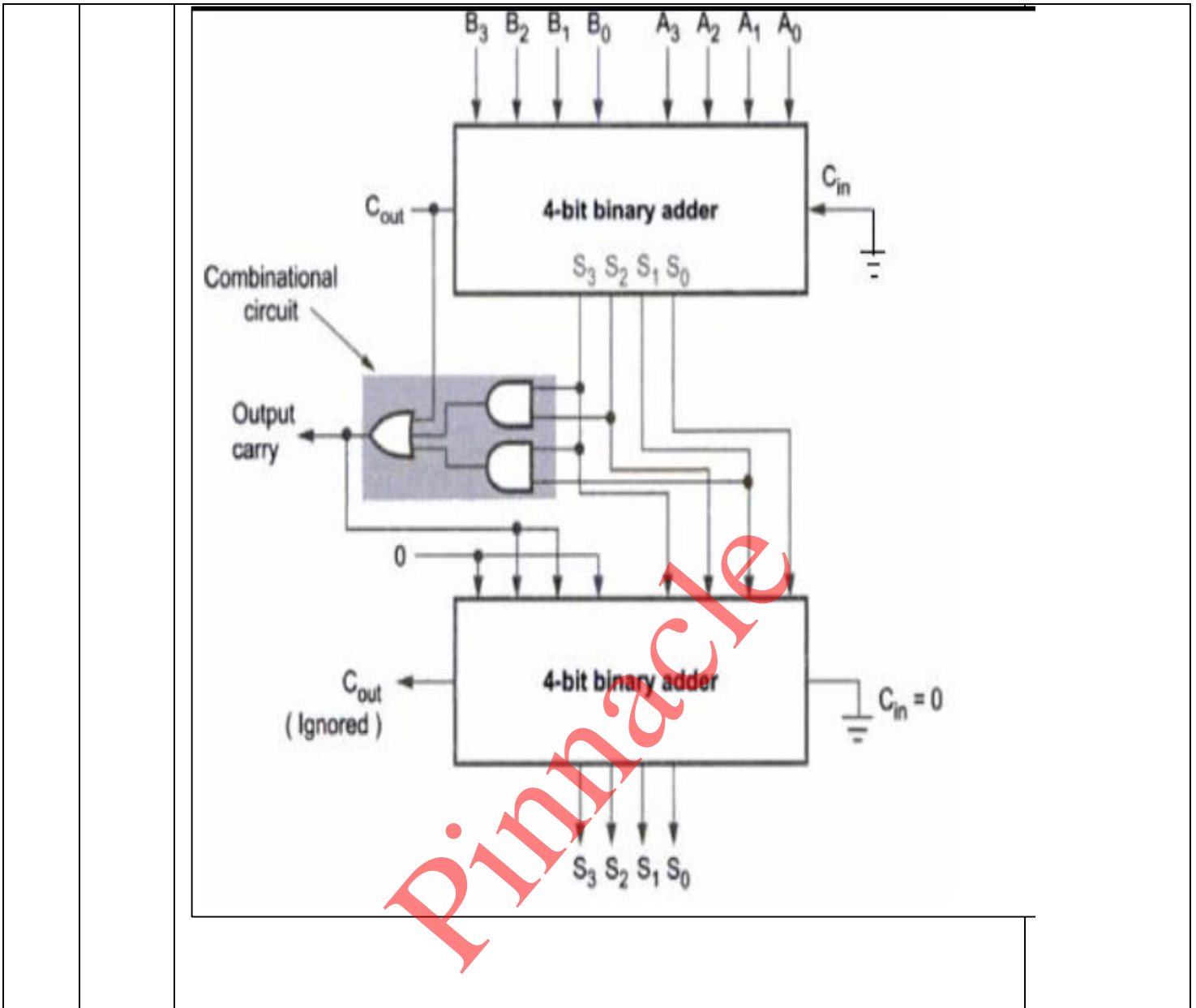

Q.5	Attempt any TWO of the following :	Total Marks 12
a)	Subtract using 2's complement method $(35)_{10} - (5)_{10}$	6M
Ans:	<p>Step 1 – Obtain binary equivalent of $(35)_{10}$ & $(5)_{10}$ & then take 2's complement of $(5)_{10}$. i.e. $(35)_{10} = (100011)_2$ $(5)_{10} = (101)_2$</p> <p>2's complement of $(5)_{10} = (000101)_2 = 111010 \rightarrow$ 1's complement + 1 ----- $(111011)_2 \rightarrow$ 2's Complement</p> <p>Step -2 :</p>	Each step 3 Marks



Now add $(100011)_2$ and $(111011)_2$

$$\begin{array}{r} 100011 \\ + 111011 \\ \hline \end{array}$$

$$\boxed{1} \quad 011110$$

→ Carry is generated so answer is in positive form, so will discard the carry generated
Therefore final answer will be $(011110)_2 = (30)_2$

b) Design a 4 bit synchronous counter and draw its logic diagram.


6M

Ans: State Table:

Present state				Next state				Flip flop inputs			
D	C	B	A	D ⁺	C ⁺	B ⁺	A ⁺	T _D	T _C	T _B	T _A
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	1
0	1	0	1	0	1	1	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	1
0	1	1	1	1	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	1
1	0	0	1	1	0	1	0	0	0	1	1
1	0	1	0	1	0	1	1	0	0	0	1
1	0	1	1	1	1	0	0	0	1	1	1
1	1	0	0	1	1	0	1	0	0	0	1
1	1	0	1	1	1	1	0	0	0	1	1
1	1	1	0	1	1	1	1	0	0	0	1
1	1	1	1	0	0	0	0	1	1	1	1


2M-State table

Kmap:

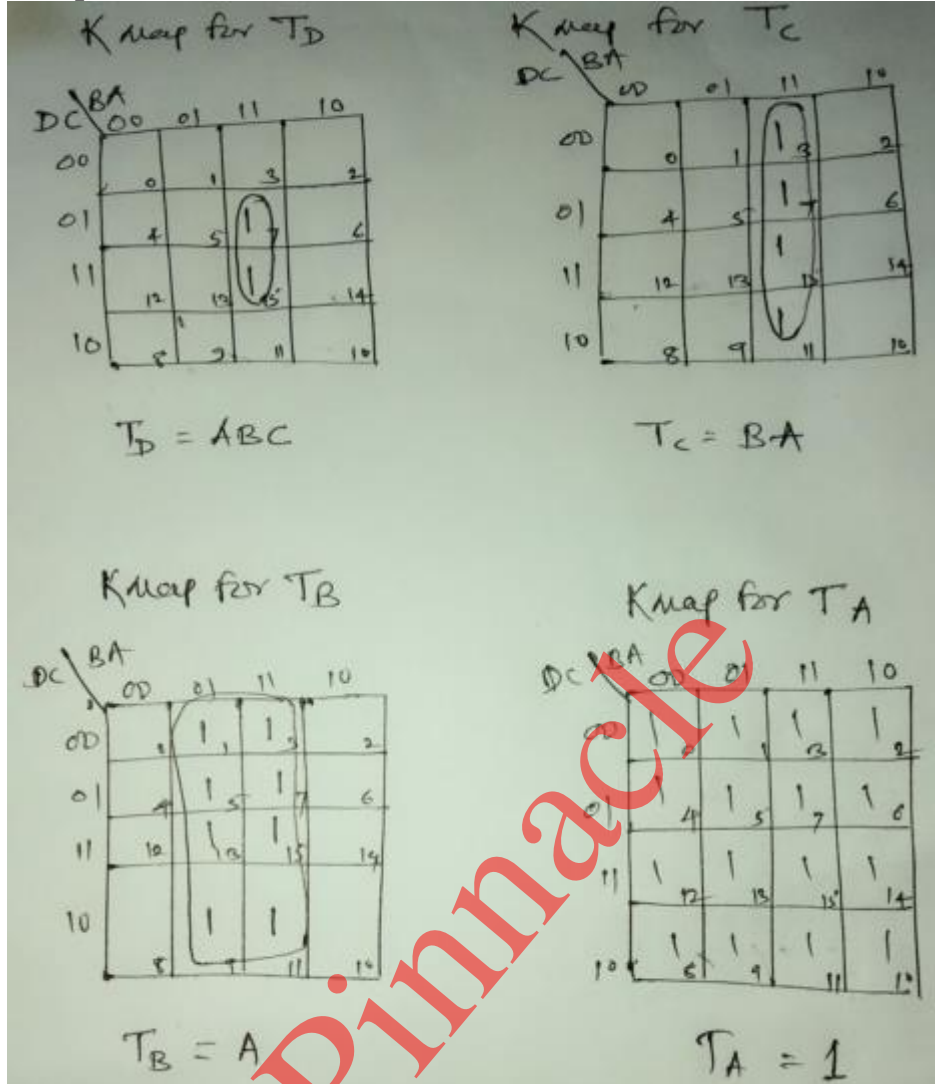

2M-Kmap

Logic Diagram:

 

2M-Logic Diagram


c)	<p>Describe the working of Successive Approximation ADC. Define Resolution and conversion time associate with ADC.</p>	6M
Ans:	<p>Circuit Diagram:</p> <p>When the start signal goes low the successive approximation register SAR is cleared and output voltage of DAC will be 0V. When start goes high the conversion starts.</p> <p>After starts, during first clock pulse the control circuit set MSB bit so SAR output will be 1000 0000. This is connected as input to DAC so output of DAC is (analog output) compared with V_{in} input voltage. If V_{DAC} is more than V_{in} the comparator output $-V_{sat}$, if V_{DAC} is less than V_{in}, the comparator output is $+V_{sat}$.</p> <p>If output of DAC i.e. V_{DAC} is $+V_{sat}$ (i.e unknown analog input voltage $V_{in} > V_{DAC}$) then MSB bit is kept set, otherwise it is reset. Consider MSB is set so SAR will contain 1000 0000.</p> <p>The next clock pulse will set next bit i.e D_6 a digital output of 1100 0000. The output voltage of DAC i.e V_{DAC} is compared with V_{in}, if it is $+V_{sat}$ the D_6 bit is kept as it is, but if it is $-V_{sat}$ the D_6 bit reset.</p> <p>The process of checking and taking decision to keep bit set or to reset is continued upto D_0.</p> <p>Then the DAC input will be digital data equal to analog input.</p> <p>When the conversation if finished the control circuits sends out an end of conversion signal and data is locked in buffer register</p>	<p>2 Marks Diagram</p> <p>2 Marks Explanation</p> <p>1 Marks Each</p>

Resolution: The voltage input change necessary for a one bit change in the output is called resolution.

Conversion Time: The conversion time is the time required for conversion from an analog input voltage to the stable digital output

OR

Circuit Diagram:

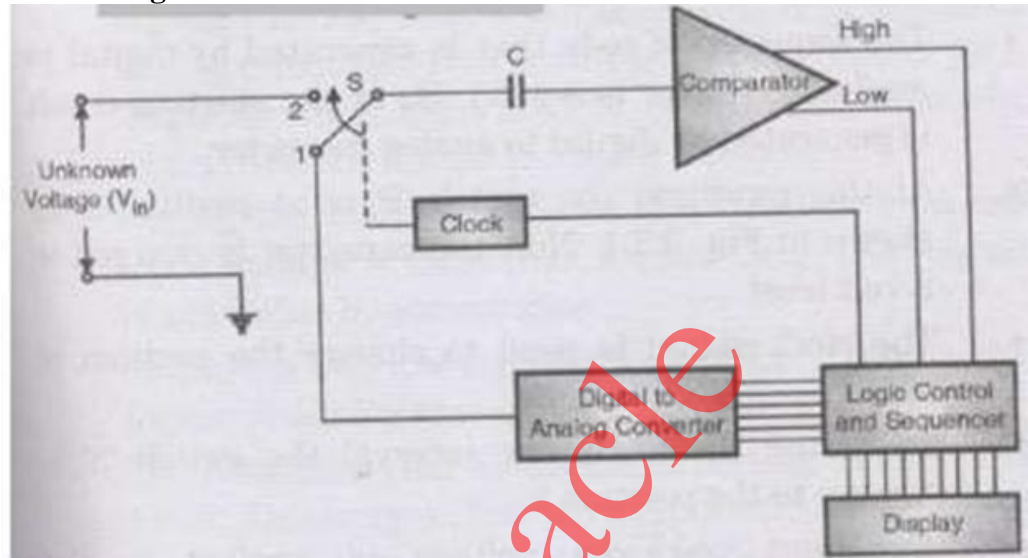

2 Marks
Diagram

Explanation:

DAC= Digital to Analog converter
EOC= End of conversion
SAR =Successive approximation register
S/H= Sample and hold circuit
 V_{in} = input voltage
 V_{ref} = reference voltage

The successive approximation Analog to Digital converter circuit typically consisting of four sub circuits-

1. A sample and hold circuit to acquire the input voltage V_{in} .
2. An analog voltage comparator that compares V_{in} to the output of internal DAC and outputs the result of comparison to successive approximation register(SAR).
3. SAR sub circuits designed to supply an approximate digital code of V_{in} to the internal DAC.
4. An internal reference DAC that supplies the comparator with an analog voltage equivalent of digital code output of SAR for comparison with V_{in} .

The successive approximation register is initialized so that most significant bit (MSB) is equal to digital 1. This code is fed into DAC which the supplies the analog equivalent of this digital code $V_{ref}/2$ into the comparator circuit for the comparison with sampled input voltage. If this analog voltage exceeds V_{in} the comparator causes the SAR to reset the bit, otherwise a bit is left as 1. Then the

2 Marks
Explanation

OUR CENTERS :

KALYAN | DOMBIVLI | THANE | NERUL | DADAR

Contact - 9136008228

next bit is set to 1 and the same test is done continuing this binary search until every bit in the SAR has been tested. The resulting code is the digital approximation of the sampled input voltage and is finally output by DAC at end of the conversion (EOC).

Resolution and conversion time associate with ADC-

Resolution:

It is the maximum number of digital output codes.

Resolution = 2^n


(OR)

It is defined as the ratio of change in the value of input analog voltage required to change the digital output by 1 LSB.

$$\therefore \text{Resolution} = \frac{V_{FS}}{2^n - 1}$$

Conversion time:

 The time difference between two instants i.e. 't₀' where SOC signal is given as input to the ADC and 't₁' where EOC signal we get as output from ADC. it should be small as possible.



1 Marks
each



Q.6	Attempt any TWO of the following:	Total Marks 12																																																																																																																																																																									
a)	Design 4 bit Binary to Gray code converter.	6M																																																																																																																																																																									
	<p>Ans:</p> <p>Truth Table for 4 bit Binary to Gray code converter</p> <table border="1" data-bbox="310 369 1276 1054"> <thead> <tr> <th colspan="4">Binary Input</th> <th colspan="4">Gray output</th> </tr> <tr> <th>B₃</th> <th>B₂</th> <th>B₁</th> <th>B₀</th> <th>G₃</th> <th>G₂</th> <th>G₁</th> <th>G₀</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table> <p>K-MAP FOR G₃:</p> <table border="1" data-bbox="324 1155 1185 1869"> <tr> <td></td> <td>B₁B₀ 00</td> <td>01</td> <td>11</td> <td>10</td> </tr> <tr> <td>B₃B₂ 00</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>01</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>11</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>10</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> </tr> </table> <p>G₃=B₃</p>	Binary Input				Gray output				B ₃	B ₂	B ₁	B ₀	G ₃	G ₂	G ₁	G ₀	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	1	0	0	1	0	0	0	1	1	0	0	1	1	0	0	1	0	0	1	0	0	0	1	1	0	0	1	0	1	0	1	1	1	0	1	1	0	0	1	0	1	0	1	1	1	0	1	0	0	1	0	0	0	1	1	0	0	1	0	0	1	1	1	0	1	1	0	1	0	1	1	1	1	1	0	1	1	1	1	1	0	1	1	0	0	1	0	1	0	1	1	0	1	1	0	1	1	1	1	1	0	1	0	0	1	1	1	1	1	1	0	0	0		B ₁ B ₀ 00	01	11	10	B ₃ B ₂ 00	0	0	0	0	01	0	0	0	0	11	1	1	1	1	10	1	1	1	1	<p>2M for truth table</p> <p>1/2m for each output equation</p> <p>2M for realization using gates</p>
Binary Input				Gray output																																																																																																																																																																							
B ₃	B ₂	B ₁	B ₀	G ₃	G ₂	G ₁	G ₀																																																																																																																																																																				
0	0	0	0	0	0	0	0																																																																																																																																																																				
0	0	0	1	0	0	0	1																																																																																																																																																																				
0	0	1	0	0	0	1	1																																																																																																																																																																				
0	0	1	1	0	0	1	0																																																																																																																																																																				
0	1	0	0	0	1	1	0																																																																																																																																																																				
0	1	0	1	0	1	1	1																																																																																																																																																																				
0	1	1	0	0	1	0	1																																																																																																																																																																				
0	1	1	1	0	1	0	0																																																																																																																																																																				
1	0	0	0	1	1	0	0																																																																																																																																																																				
1	0	0	1	1	1	0	1																																																																																																																																																																				
1	0	1	0	1	1	1	1																																																																																																																																																																				
1	0	1	1	1	1	1	0																																																																																																																																																																				
1	1	0	0	1	0	1	0																																																																																																																																																																				
1	1	0	1	1	0	1	1																																																																																																																																																																				
1	1	1	0	1	0	0	1																																																																																																																																																																				
1	1	1	1	1	0	0	0																																																																																																																																																																				
	B ₁ B ₀ 00	01	11	10																																																																																																																																																																							
B ₃ B ₂ 00	0	0	0	0																																																																																																																																																																							
01	0	0	0	0																																																																																																																																																																							
11	1	1	1	1																																																																																																																																																																							
10	1	1	1	1																																																																																																																																																																							



	B1B0	00	01	11	10
B3B2	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	1	1	1	1

K-MAP FOR G2:

$$G2 = \overline{B3} B2 + \overline{B2} B3$$

$$= B3 \text{ XOR } B2$$

K-MAP FOR G1:

	B1B0	00	01	11	10
B3B2	00	0	0	1	1
	01	1	1	0	0
	11	1	1	0	0
	10	0	0	1	1

OUR CENTERS :

KALYAN | DOMBIVLI | THANE | NERUL | DADAR

Contact - 9136008228

$$G1 = \overline{B2} B1 + B2 \overline{B1}$$

$$= B1 \text{ XOR } B2$$


K-MAP FOR G0:

	B1B0	00	01	11	10
B3B2	00	0	1	0	1
	01	0	1	0	1
	11	0	1	0	1
	10	0	1	0	1

$$G0 = \overline{B1} B0 + B1 \overline{B0}$$

$$= B1 \text{ XOR } B0$$

Diagram for 4 bit Binary to Gray code converter:

 

Note: Realization of output equations can be done using Basic or Universal gates



	<p>b) Compare the following (Any three points)</p> <p>i) Volatile with Non-volatile memory</p> <p>ii) SRAM with DRAM memory</p>	6M																																							
	<p>Ans:</p> <table border="1" data-bbox="310 342 1338 898"> <thead> <tr> <th>Parameter</th> <th>Volatile memory</th> <th>Non-Volatile memory</th> </tr> </thead> <tbody> <tr> <td>definition</td> <td>Memory required electrical power to keep information stored is called volatile memory</td> <td>Memory that will keep storing its information without the need of electrical power is called nonvolatile memory.</td> </tr> <tr> <td>classification</td> <td>All RAMs</td> <td>ROMs, EPROM, magnetic memories</td> </tr> <tr> <td>Effect of power</td> <td>Stored information is retained only as long as power is on.</td> <td>No effect of power on stored information</td> </tr> <tr> <td>applications</td> <td>For temporary storage</td> <td>For permanent storage of information</td> </tr> </tbody> </table> <p>2. SRAM with DRAM memory</p> <table border="1" data-bbox="310 1010 1338 1499"> <thead> <tr> <th>Parameter</th> <th>SRAM</th> <th>DRAM</th> </tr> </thead> <tbody> <tr> <td>Circuit configuration</td> <td>Each SRAM cell is a flip flop</td> <td>Each cell is one MOSFET & a capacitor</td> </tr> <tr> <td>Bits stored</td> <td>In the form of voltage</td> <td>In the form of charges</td> </tr> <tr> <td>No of components per cell</td> <td>More</td> <td>Less</td> </tr> <tr> <td>Storage capacity</td> <td>Less</td> <td>More</td> </tr> <tr> <td>Refreshing</td> <td>It does not require refreshing</td> <td>It require refreshing.</td> </tr> <tr> <td>Cost</td> <td>It is expensive</td> <td>It is cheaper</td> </tr> <tr> <td>Speed</td> <td>It is faster</td> <td>It is slower comparatively</td> </tr> </tbody> </table>	Parameter	Volatile memory	Non-Volatile memory	definition	Memory required electrical power to keep information stored is called volatile memory	Memory that will keep storing its information without the need of electrical power is called nonvolatile memory.	classification	All RAMs	ROMs, EPROM, magnetic memories	Effect of power	Stored information is retained only as long as power is on.	No effect of power on stored information	applications	For temporary storage	For permanent storage of information	Parameter	SRAM	DRAM	Circuit configuration	Each SRAM cell is a flip flop	Each cell is one MOSFET & a capacitor	Bits stored	In the form of voltage	In the form of charges	No of components per cell	More	Less	Storage capacity	Less	More	Refreshing	It does not require refreshing	It require refreshing.	Cost	It is expensive	It is cheaper	Speed	It is faster	It is slower comparatively	<p>Any 3points (each 1 mark)</p>
Parameter	Volatile memory	Non-Volatile memory																																							
definition	Memory required electrical power to keep information stored is called volatile memory	Memory that will keep storing its information without the need of electrical power is called nonvolatile memory.																																							
classification	All RAMs	ROMs, EPROM, magnetic memories																																							
Effect of power	Stored information is retained only as long as power is on.	No effect of power on stored information																																							
applications	For temporary storage	For permanent storage of information																																							
Parameter	SRAM	DRAM																																							
Circuit configuration	Each SRAM cell is a flip flop	Each cell is one MOSFET & a capacitor																																							
Bits stored	In the form of voltage	In the form of charges																																							
No of components per cell	More	Less																																							
Storage capacity	Less	More																																							
Refreshing	It does not require refreshing	It require refreshing.																																							
Cost	It is expensive	It is cheaper																																							
Speed	It is faster	It is slower comparatively																																							


c) Give block schematic of decade counter IC 7490. Design Mod-7 counter using this IC.

6M

Ans:

1. block schematic of decade counter IC 7490-

2M block schematic

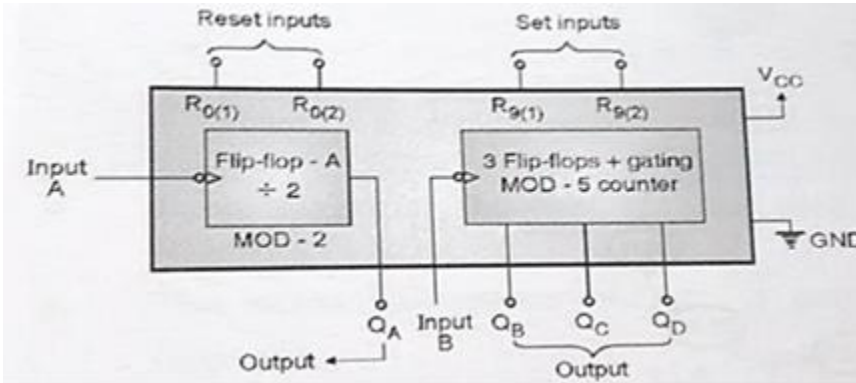

Mod-7 means states are from 0,1,2,3,4,5,6,0

Therefore we have to reset counter IC 7490 when $Q_D, Q_C, Q_B, Q_A = 0111$

Design reset logic:

Output of reset circuit should be HIGH because $R_0(1)$ and $R_0(2)$ are active high inputs.

Therefore reset logic output should be low for states 0 to 6.

Output should be HIGH for states 7 onwards.


Truth table & K-map:

Q_D	Q_C	Q_B	Q_A	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1

} Invalid State

For Y

Truth Table-1M
Kmap-1M
Logical Dig-2M

 

Expression for Y:

$$Y = Q_C Q_B Q_A + Q_D$$

Circuit is-



Logic Diagram:

